



KISII UNIVERSITY

UNIVERSITY EXAMINATIONS

SECOND YEAR EXAMINATION FOR THE AWARD OF THE DEGREE OF BACHELOR OF SCIENCE IN COMPUTER SCIENCE AND SOFTWARE ENGINEERING

FIRST SEMESTER 2021/2022
(FEBRUARY – JUNE, 2022)

PHYS 213: INTRODUCTION TO ELECTRONICS

STREAM: Y2 S1

TIME: 2 HOURS

DAY: WEDNESDAY, 12:00 PM – 2:00 PM

DATE: 11/05/2022

INSTRUCTIONS

- 1. Do not write anything on this question paper.***
- 2. Answer Question ONE and any other TWO questions.***

QUESTION ONE (30 MARKS)


- Explain the superposition theorem (4 marks)
- Differentiate between active filters and passive filters (4 marks)
- A filter section is required to pass all frequencies above 25 kHz and to have a nominal impedance of 600Ω . Design;
 - a high-pass T-section filter, and (6 marks)
 - a high-pass π -section filter to meet these requirements. (6 marks)
- A transistor has $\beta_{dc} = 150$ and $I_B = 75\mu A$. Calculate I_c (4 marks)

- e) Explain the following
- i. Attenuation (2 marks)
 - ii. Two port networks (2 marks)
 - iii. cut-off frequency (2 marks)

QUESTION TWO (20 MARKS)

- a) Explain the voltage ampere characteristic curve of a diode using an appropriate diagram. (6 marks)

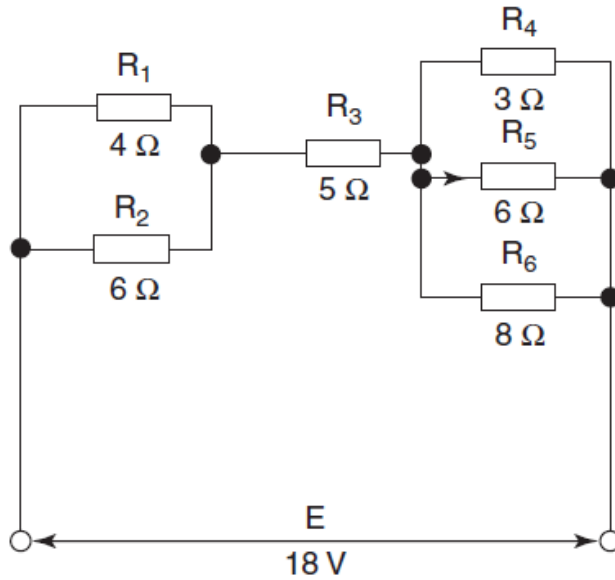- b) For the circuit shown below calculate;
- (i) the current drawn from the source,
 - (ii) the p.d. across each resistor,
 - (iii) the current through each resistor, and
 - (iv) the power dissipated by the 5 Ω resistor.




(8 marks)

- c) Calculate f_{max} for an op-amp that has an S_R of $5V/\mu s$ and a peak output voltage of 10V. Also comment about its slew rate distortion.

(6 marks)


QUESTION THREE (20 MARKS)

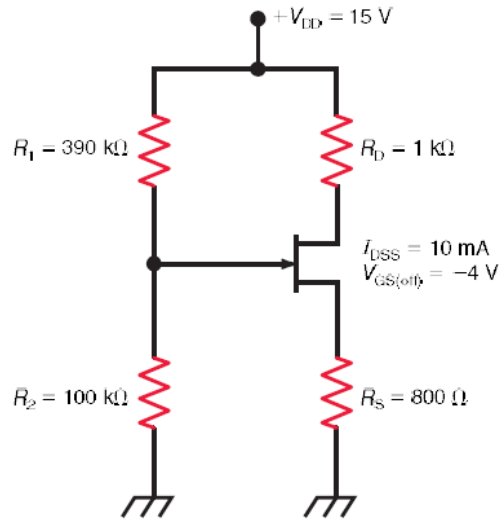- a) In the voltage divider bias JFET circuit below, $V_{GS} = -1 V$, Calculate V_G , V_S , I_D and V_D .



(10 marks)

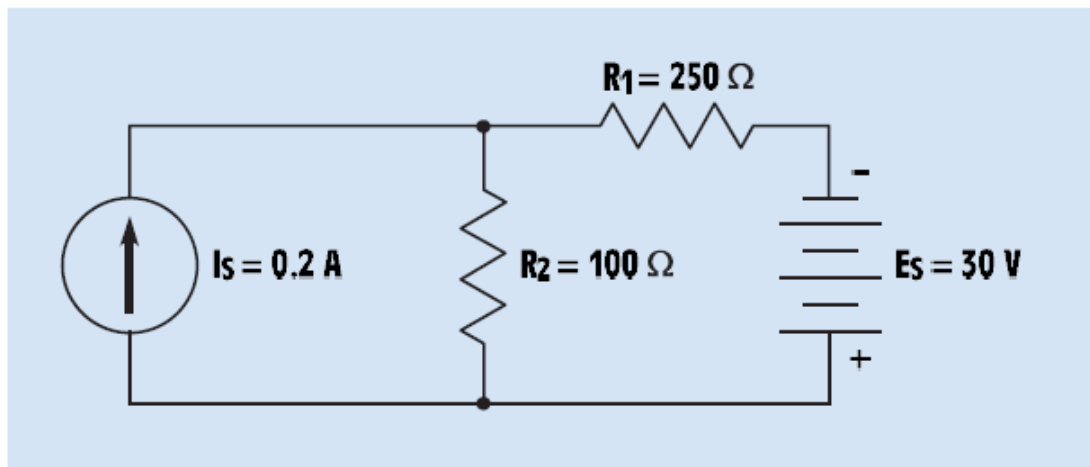- b) The circuit below contains a voltage source of 30V and a current source of 0.2A. Calculate the amount of current flowing through R2




(10 marks)

QUESTION FOUR (20 MARKS)

- a) Using the second diode approximation, for the figure below, calculate the following;

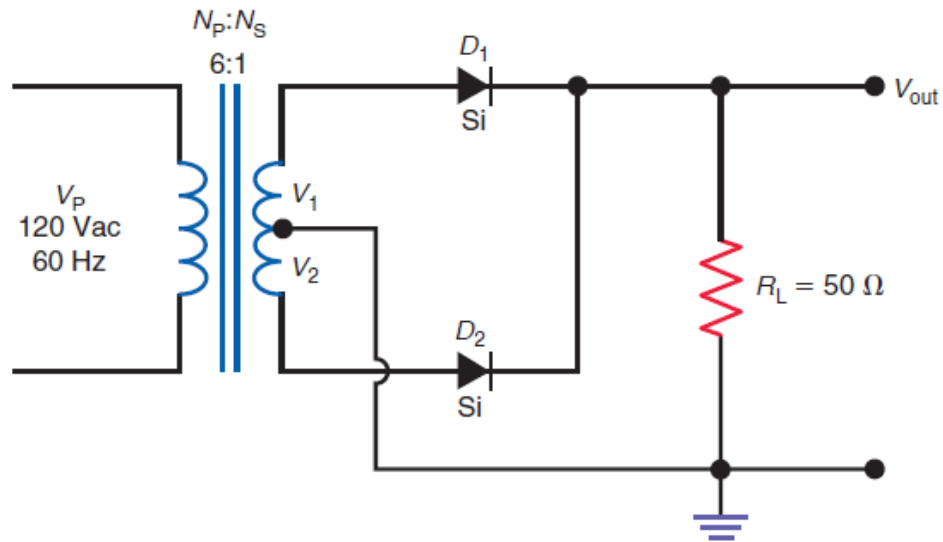- i. $V_{out(pk)}$
- ii. V_{dc}
- iii. I_L
- iv. I_{diode}
- v. PIV for D_1 and D_2 , and
- vi. f_{out} .



(10 marks)

b) Explain the working of a half wave rectifier.

(4 marks)

c) Explain the characteristics and purpose of each of the following regions in a transistor:

- i. emitter.
- ii. base.
- iii. collector.


(6 marks)

QUESTION FIVE (20 MARKS)

a) Explain the process of doping a semiconductor to produce an n-type and p-type material.

(4 marks)

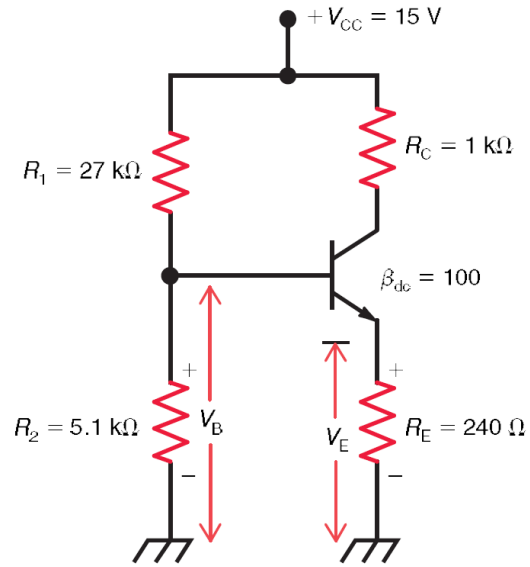b) For the voltage divider bias circuit shown in the figure below, solve for V_B , V_E , I_C , V_C and V_{CE} . Also, calculate $I_{C(sat)}$ and $V_{CE(off)}$. Finally, construct a dc load line showing the values of $I_{C(sat)}$, $V_{CE(off)}$, I_{CQ} and V_{CEQ} .



- c) Distinguish between a low pass and high pass filters. (12 marks)
- (4 marks)