



KISII UNIVERSITY

UNIVERSITY EXAMINATIONS

SECOND YEAR EXAMINATION FOR THE AWARD OF THE DEGREE OF BACHELOR OF SCIENCE IN INFORMATION TECHNOLOGY

SECOND SEMESTER 2023/2024

[JAN – APRIL, 2024]

COMP 201: BASIC CIRCUIT SYSTEMS

STREAM: Y2 S2

TIME: 2 HOURS

DAY: FRIDAY, 12:00 - 2:00 P.M.

DATE: 19/04/2024

INSTRUCTIONS

- 1. Do not write anything on this question paper.**
- 2. Answer question ONE (Compulsory) and any other TWO questions.**

QUESTION ONE

- a. Briefly explain the following terms as used in basic circuit design
- Digital system (2 marks)
 - Basic latch (2 marks)
 - Boolean algebra (2 marks)
- b. Discuss the following types of Error – Detecting codes
- Checksums (3 marks)
 - Parity (3 marks)
 - Block parity (3 marks)
- c. (i) Explain five characteristics of digital system (5 marks)
- (ii) Briefly explain four advantages of digital system over Analog system (4 marks)
- e. Simplify $F = x'yz + x'yz' + xz$ (3 marks)
- f. Draw a truth table for F1 where $F1 = x + y'z$ (4 marks)

QUESTION ON TWO

a. Write short notes on the following:

- i. Decimal numbers (3 marks)
 - ii. Binary numbers (3 marks)
 - iii. Octal numbers (3 marks)
 - iv. Hexadecimal numbers (3 marks)
- b. Use two's complement to perform the following arithmetic operation (4 marks)
- c. Differentiate between a full adder and half adder. (4 marks)

QUESTION ON THREE

- a. By the help of a diagram discuss a combinational circuit and list its design procedure. (8mks)
- b. By the help of graphical symbols explain the following types of gates
- i. AND (3mks)
 - ii. OR (3mks)
 - iii. NOR (3mks)
 - iv. NAND (3mks)

QUESTION FOUR

- a. Explain capabilities of a general shift register. (6 marks)
- b. Memory structures are crucial in digital design. Discuss the following types of memories used in basic circuit design.
- (i) PROM (2 marks)
 - (ii) EPROM (2 marks)
 - (iii) SRAM (2 marks)
 - (iv) DRAM (2 marks)
- c. Briefly explain how communication is achieved between memory and its environment. (6 marks)

QUESTION FIVE

- a. Express the Boolean function $F = A + B'C$ as a sum of minterms (4 marks)
- b. Express the Boolean function $F = xy + x'z$ as a product of maxterms. (4 marks)
- c. (i) List two limitations of Karnaugh maps (2 marks)
(ii) Reduce the expression $f=(A+B)(A+B')(A'+B')$ using mapping (5 marks)
- d. Prove that $x'y'z' + x'yz' + xyz' = x'z' + yz'$ (5 marks)